

ECE 150 Homework 1

Fall 2022.

Due September 28th before class.

Hand in submission in person or upload as a PDF to MS Teams.

Show all work for any credit.

- Convert 42_{10} to:
 - Base 2
 - Base 5
 - Base 16
- Convert the following values to base 10
 - 10111001_2
 - 4213_5
 - $D3B_{16}$
- Convert $E17_{16}$ to binary and octal without converting to base 10.
- Perform the addition $32_{10} + 23_{10}$ in binary.
- Perform the subtraction $23_{10} - 32_{10}$ in binary.
- Use Boolean Algebra to simplify these equations:
 - $W = \overline{A}\overline{B}C + BC + A\overline{B}C$
 - $X = \overline{A}BC + \overline{B} + C$
 - $Y = \overline{A}B + C + ABC$
 - $Z = \overline{AC} + \overline{B} + C$
- Given the circuit in Figure 1
 - Write the Boolean function for F.
 - Fill out the truth table, showing intermediate nodes if needed.
 - Simplify the expression using a Karnaugh map.
 - Use the simplified expression to draw a sum of products implementation of the circuit

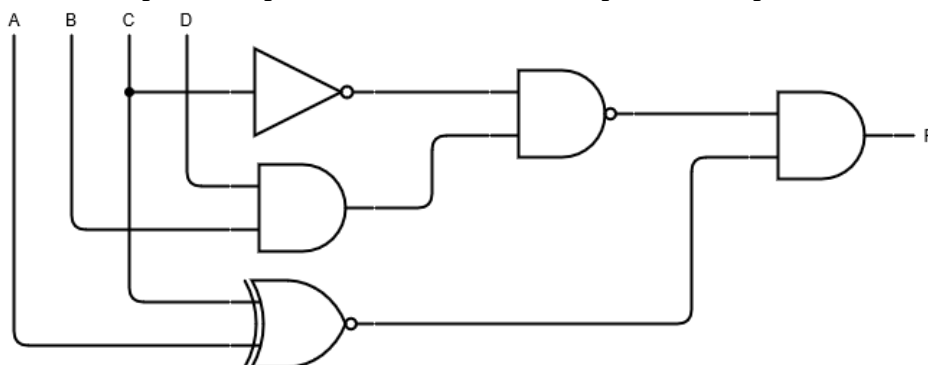


Figure 1

- From the truth table below:

- a. Write the sum of minterms expression for F (direct from the table)
- b. Using a Karnaugh map find a simplified expression for F
- c. Draw a diagram of the simplified expression as a sum of products circuit

A	B	C	D	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1